Homework 5_ ECE 1238 Rayan Hassan

$$\Rightarrow 0.05 = 1.1 - 0.52 + \frac{1}{2 k_0} - \sqrt{(1.1 - 0.52 + \frac{1}{2 k_0})^2 - \frac{2 \times 1.1}{2}}$$

$$= 0.53 + \frac{1}{2k_0} - \sqrt{0.58 + \frac{1}{2k_0}^2 - \frac{1.1}{k_0}}$$

$$\Rightarrow \sqrt{(0.58 + \frac{1}{2 k_0})^2 - \frac{1.1}{k_0}} = 0.53 + \frac{1}{2 k_0}$$

$$(0.58 + \frac{1}{2k_0})^2 - \frac{1.1}{k_0} = (0.53 + \frac{1}{2k_0})^2$$

$$\Rightarrow 0.58^{2} + \frac{0.58}{k_{0}} + \frac{1}{4/k_{0}^{2}} - \frac{1.1}{k_{0}} = 0.53^{2} + \frac{0.53}{k_{0}} + \frac{1}{4/k_{0}^{2}}$$

$$\Rightarrow 0.58^2 - \frac{0.52}{k_0} = 0.53^2 + \frac{0.53}{k_0}$$

$$\Rightarrow 0.58^2 - 0.53^2 = \frac{1.05}{k_0}$$

$$\Rightarrow 0.0555 = \frac{1.05}{k_0}$$

$$\Rightarrow k_{n} = \frac{1.05}{0.0555} \Rightarrow k_{n} = 18.92$$

$$mA/v^{2}$$

$$I_{R} = I_{0}$$

$$\frac{V_{DO} - V_{0L}}{R_{L}} = \frac{1}{2} K_{0}' \frac{W}{L} \left(V_{GS} V_{0}\right)^{2}$$

$$\frac{V_{DO} - V_{0L}}{R_{L}} = \frac{1}{2} K_{0}' \frac{W}{L} \left(V_{GS} V_{0}\right)^{2}$$

$$\frac{V_{DO}}{R_{L}} = \frac{1}{2} K_{0}' \frac{W}{L} \left(V_{CS} V_{0}\right)^{2}$$


$$\frac{V_{DO}}{R_{L}} = \frac{1}{2} K_{0} \frac{W}{L} \left(V_{CS} V_{0}\right)^{2}$$

$$\frac{V_{DO}}{R_{L}} = \frac{1}{2} K_{0} \frac{W}{L} \left(V_{CS} V_{0}\right)^{2}$$


>
$$\frac{\omega}{L} = \frac{0.525}{0.044 \times 0.3364} = \frac{\omega}{L} \approx 35.47$$

1) (b)


Circuit

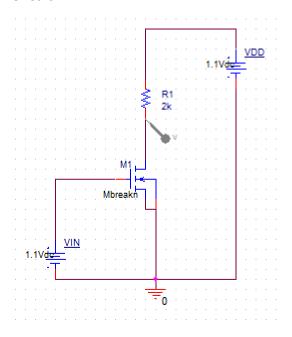

Pspice model

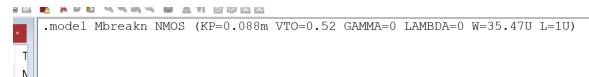

General curve

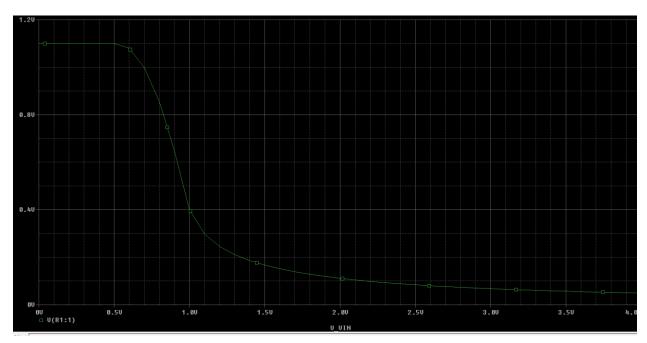

Report

```
*** Creating circuit file "UYFKC cir"
*** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT SIMULATIONS

**Libraries:
** Local Libraries:
** Local Libraries:
** From [PSPICE NETLIST] section of C:\Users\RAYAN\AppData\Roaming\SPB_Data\cdssetup\OrCAD_PSpice\17.2.0\PSpice.ini file:
11b "nond.lib"

**Analysis directives:
DC LIN 'VIN 04 0.1
OPPTIONS ADVOOW
PROBE64 (Valias(*)) I(alias(*)) W(alias(*)) D(alias(*)) NOISE(alias(*))
INC "..\SCHEMATIC1.net"

***** INCLUDING SCHEMATIC1.net ****
** source IUWR
R. RI
***** M00123 N00127 2k TC=0.0
VUN N00127 0 1 1Vdc
VUN N00127 0 1 1Vdc
VUN N00127 0 10 1Vdc
VUN N00127 0 1 1Vdc
V
```

```
Mbreakn
          NMOS
 LEVEL
            1.000000E-06
     I.
W
          35.470000E-06
.52
   VTÖ
    ŔĎ
          88.000000E-06
 GAMMA
           0
           , 6
0
   PHI
LAMBDA
    IS
JS
          10.000000E-15
           -0
    PΒ
  PBSV
             . 8
  CJŚW
  CGSO
  CGDO
            n
  CGBO
   TOX
    x_{J}
          10.000000E+03
 UCRIT
DIOMOD
  VFB
LETA
            n
  WETA
            ō
    ŪΟ
  TEMP
   VDD
 XPART
```

```
JOB CONCLUDED
```

*** 10/20/21 03:11:48 ****** PSpice Lite (March 2016) ****** ID# 10813 ****

1) (C)


Using the cursor, I found:

VOH \approx 1.089 V, VIL \approx 0.612 V

 $VOL \approx 0.389 \text{ V, VIH} \approx 1.034 \text{ V}$

$$NML = VIL - VOL = 0.612 - 0.389 = 0.223 V$$


2) (a)

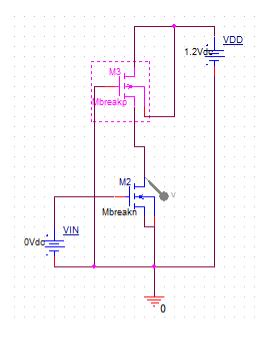


.model Mbreakn NMOS (KP=94.3U VTO=0.58 W=12U L=1U UO=42.8636 LD=4.00E-8 VSAT=124340)


.model Mbreakn NMOS (KP=94.3U VTO=0.58 W=12U L=1U UO=42.8636 LD=4.00E-8 VSAT=124340)

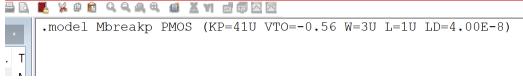.model Mbreakn NMOS (KP=41U VTO=-0.56 W=3U L=1U LD=4.00E-8)



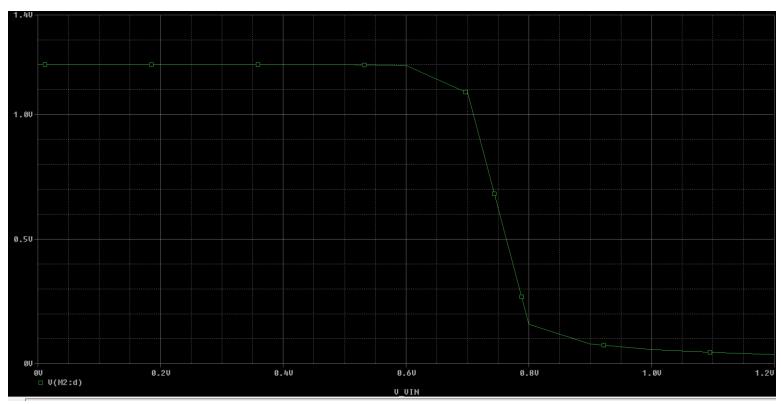


```
Mbreakn
NMOS
                                               Mbreakp
PMOS
            LEVEL
                                               1
1.000000E-06
3.000000E-06
40.000000E-09
                        1.000000E-06
12.000000E-06
40.000000E-09
               LĎ
VTO
KP
                                               -.56
41.000000E-06
                        94.300000E-06
            GAMMA
PHI
                                                   . 6
                       .6
0.000000E-15
0.8
.8
          LAMBDA
IS
JS
PB
PBSW
CJ
CJSW
                                               0.000000E-15
                                                   8
           CJSW
CGSO
CGDO
CGBO
TOX
XJ
UO
UCRIT
DIOMOD
VFB
                        42.8636
10.000000E+03
                                               10.000000E+03
             VFB
VETA
UO
TEMP
VDD
            XPART
VSAT
                       124.340000E+03
                JOB CONCLUDED
  **** 10/20/21 04:35:15 ****** PSpice Lite (March 2016) ****** ID# 10813 ****
    ** Profile: "SCHEMATIC1-RG" [ C:\Users\RAYAN\AppData\Roaming\SPB_Data\kjqwed-PSpiceFiles\SCHEMATIC1\RG .sim ]
                JOB STATISTICS SUMMARY
RG det (ect... P RG out.1
```

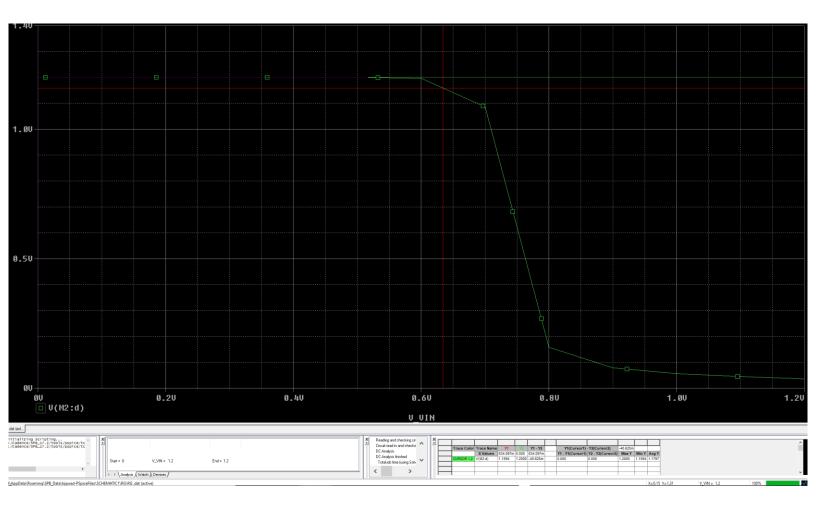

From this we see that:

VOH = 1.194 V and VIL = 0.634097V

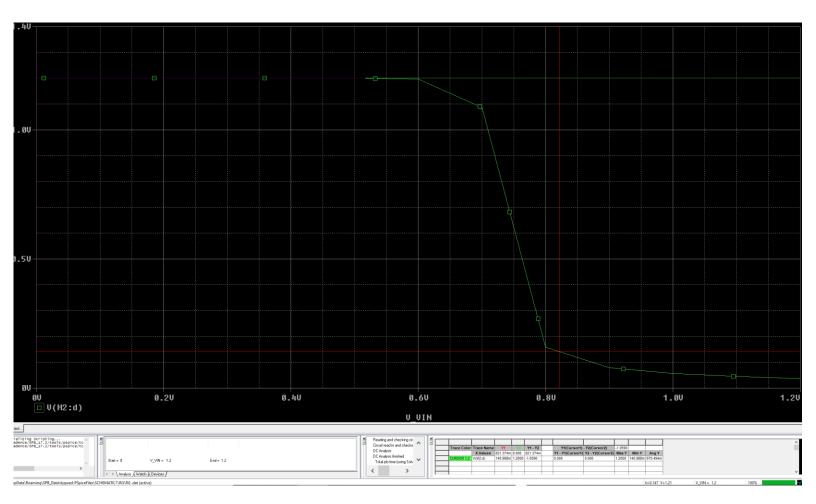

From this we see that:

VOL = 0.14V and VIH = 0.82137V

$$NML = VIL - VOL = 0.634097 - 0.14 = 0.4941 V$$

(b) Results are almost the same as the ones in the calculations